



INSTITUT  
Mines-Télécom

# Amplification

## Electronique des Systèmes d'Acquisition ELEC 101



Site web: <http://perso.telecom-paristech.fr/jabbour/enseignement/elec101/>



# Plan

## ■ Amplifier


- Large signal and small signal
- Performance indices
- Exercises

## ■ Operational amplifier



- Performance indices
- Feedback
- Exercises
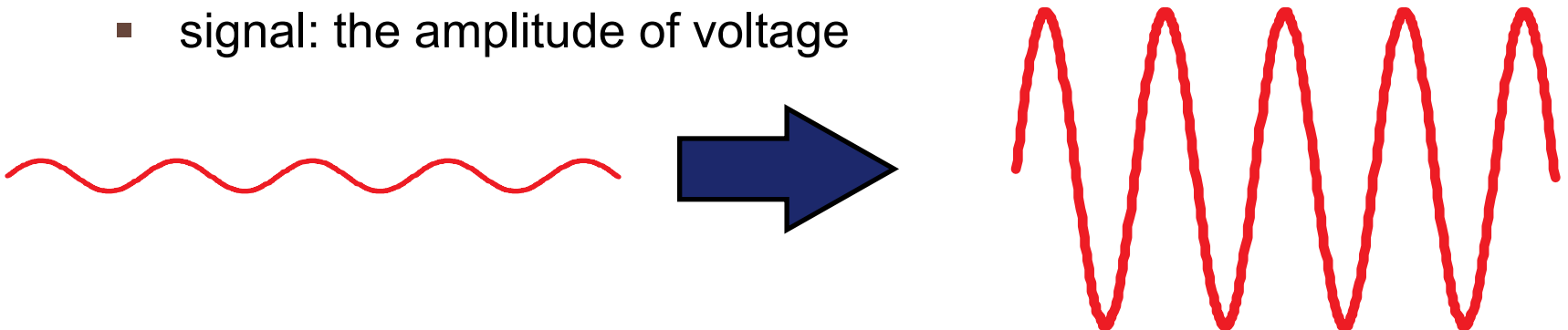
# Information, Signal, Amplification



- **Information** is carried by the **variation** of electrical signal
- **Signal** : current, voltage, charge quantity, electrical magnetical fields.
- **Variable carrier of information** : **amplitude**, frequency, or phase
- **Objectives of the amplification function**
  - **Linear** amplification (without deformation)
  - Of a variable signal (speech, sound, image, radio, video)
  - signal: the amplitude of voltage




# Amplification in digital world

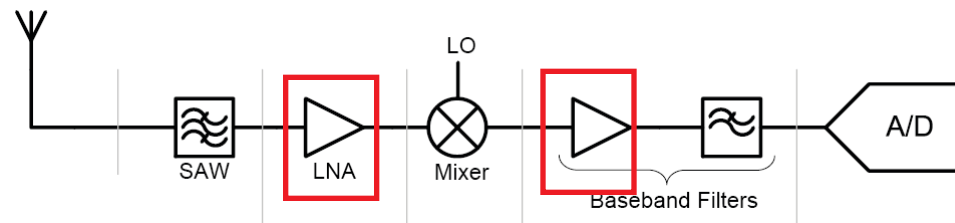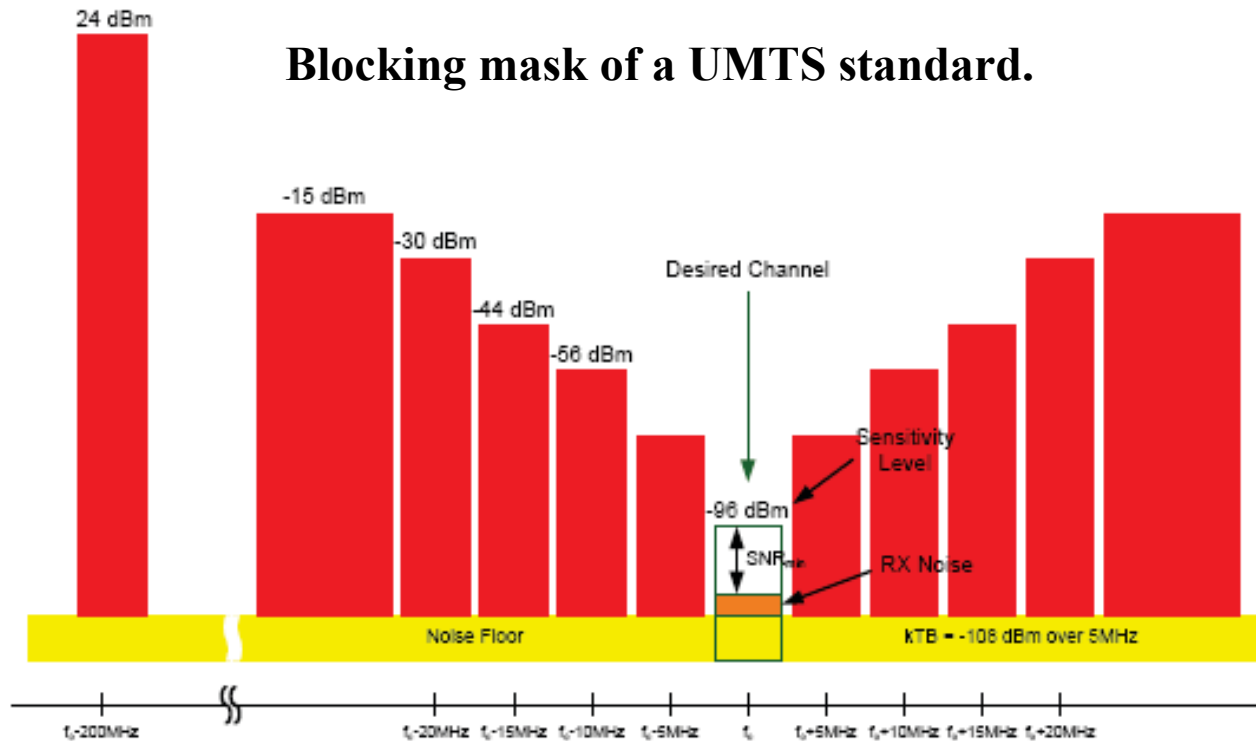

# Amplification in digital world

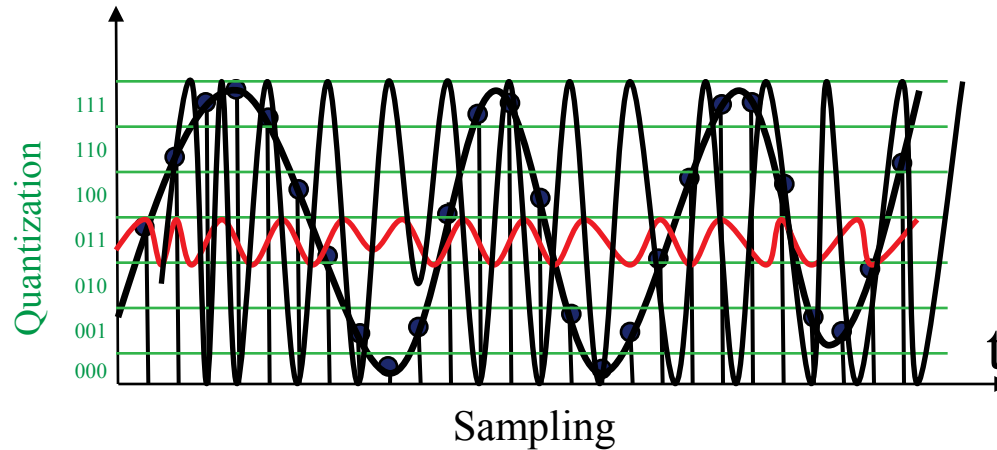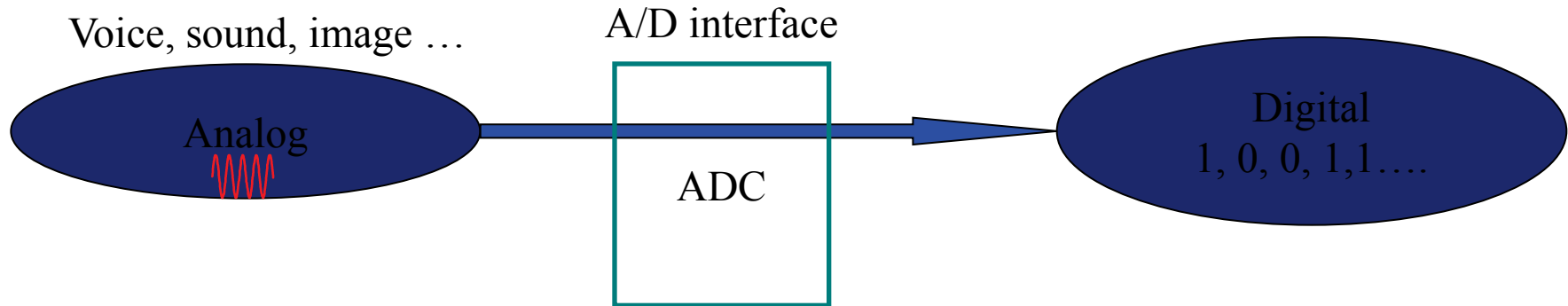


# Amplification

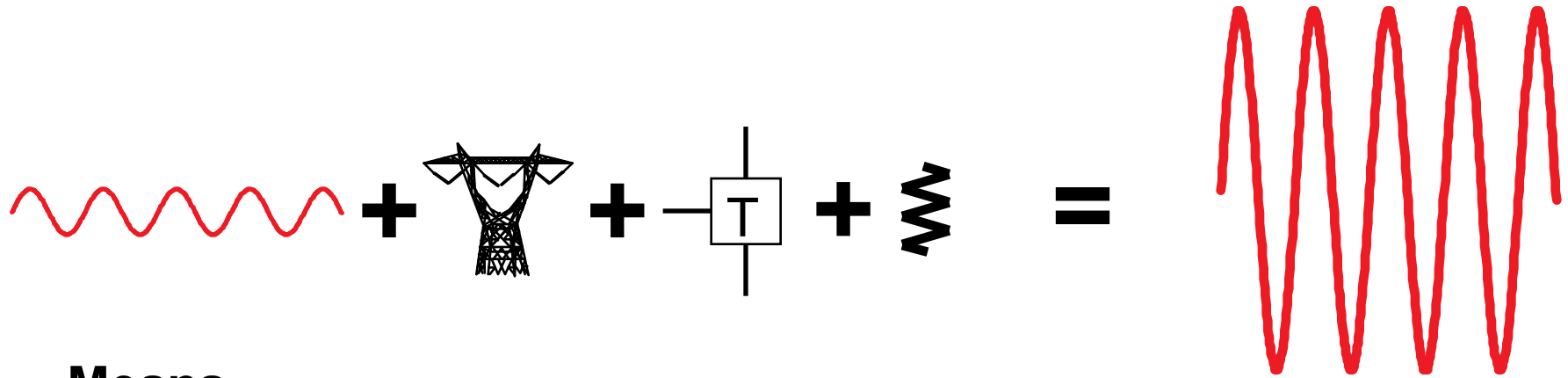

Means

- Energy resource (dc voltage)
- Modulator of current driven by voltage (transistor)
- Current/voltage converter (load resistance)

# Amplifier : basic circuit

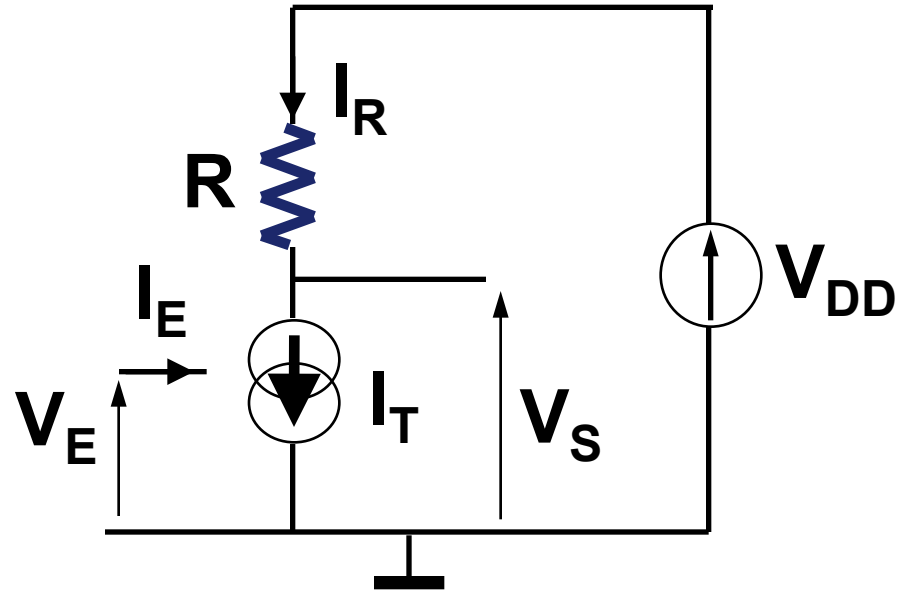


- Energy resource :  $V_{DD} \rightarrow I_R, I_T$
- Modulator of current :  $I_T = f(V_E)$
- Current/voltage converter :  $V_S = g(I_T)$
- Gain
- Linearity
- Bandwidth

# Basic amplifier
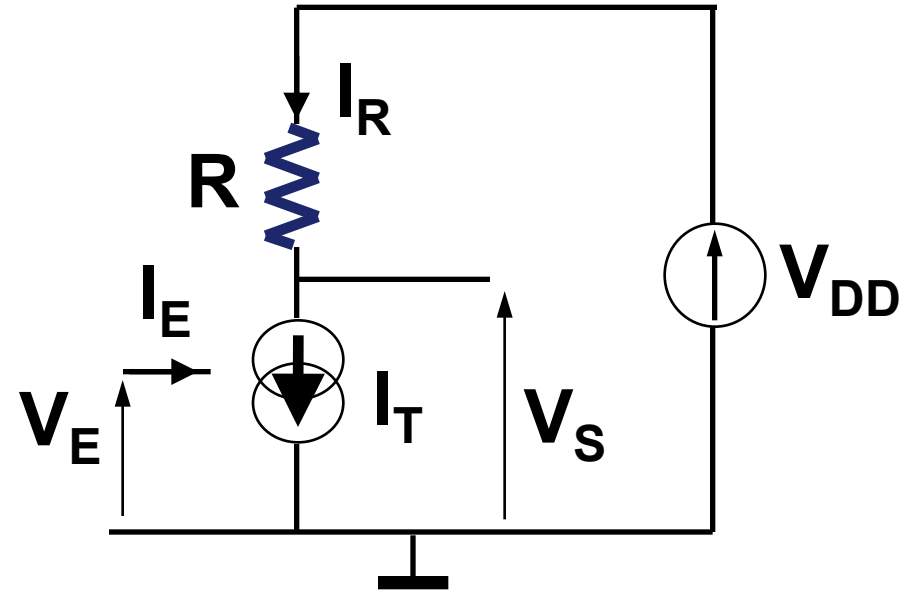
## ➤ Ideal

- $I_T = g_m \cdot V_E$
- $V_S = V_{DD} - R \cdot I_R$
- $V_S = V_{DD} - R \cdot g_m \cdot V_E$

$$\text{Gain} = \partial V_S / \partial V_E = -R \cdot g_m$$



## ➤ Reality

- $I_T = f(V_E)$  : Non linear function
- i.e. :  $I_T = K \cdot (V_E - V_T)^2$

## ➤ How to determine performance? -> what kind of analysis?



# Transfer function

- **Transfer function**

  - ⇒ Non linear

- **Local linearization**

- $V_S - V_{S0} \approx G \cdot (V_E - V_{E0})$


- $v_s \approx G \cdot v_e$

- **G depend on  $M_0$**

- **$M_0$  : operation point**

- **To determine operation point  $M_0$**

  - Static analysis

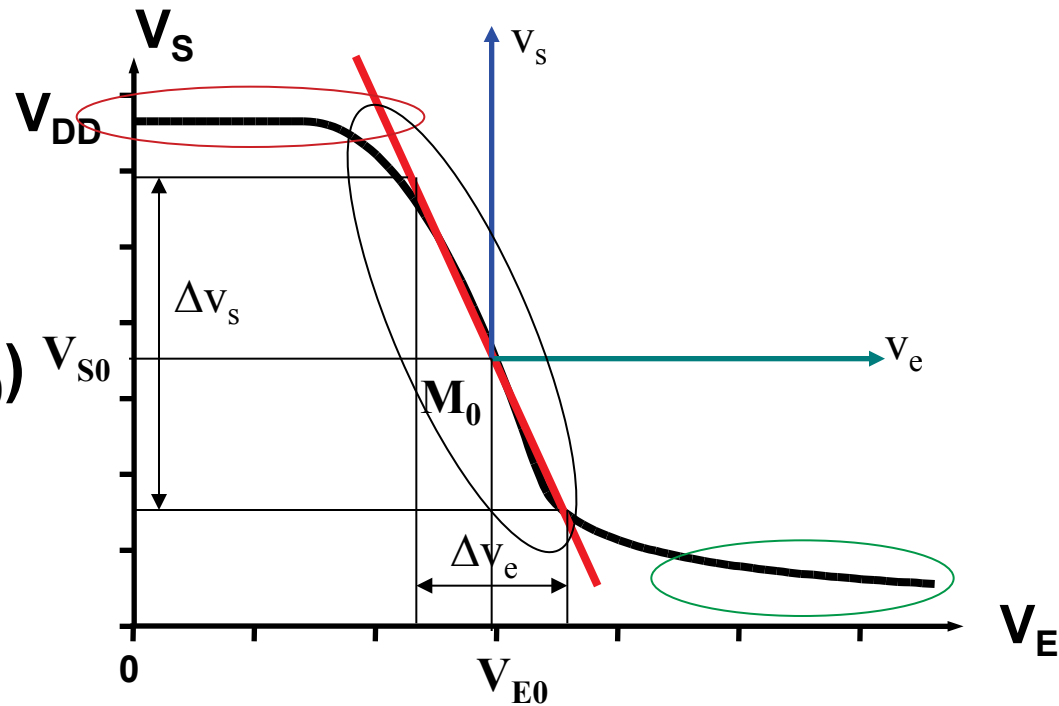

# Analysis types

## ■ Static analysis

- Parameters of the operation point ( $M_0$ )

## ■ Large signal analysis

- Transfer function
- Maximal excursions
- Distortion ratio
- Operation point

## ■ Small signal analysis « linear analysis »

- Gain, input and output resistances

## ■ Harmonic analysis

- Linear analysis + capacitors [  $Z(c) = \frac{1}{j\omega C}$  ]
- Complex gain, bandwidth

# Large signal


## Static and large signal analysis

- Transfer function
- Static gain :  $A_0$
- Offset
- Input dynamic
- Output dynamic
- Saturation
- Slew-rate

$$Q = V \cdot C$$





$$I = dQ/dt = C \cdot dV/dt$$

$$dV/dt = I/C < I_0/C$$

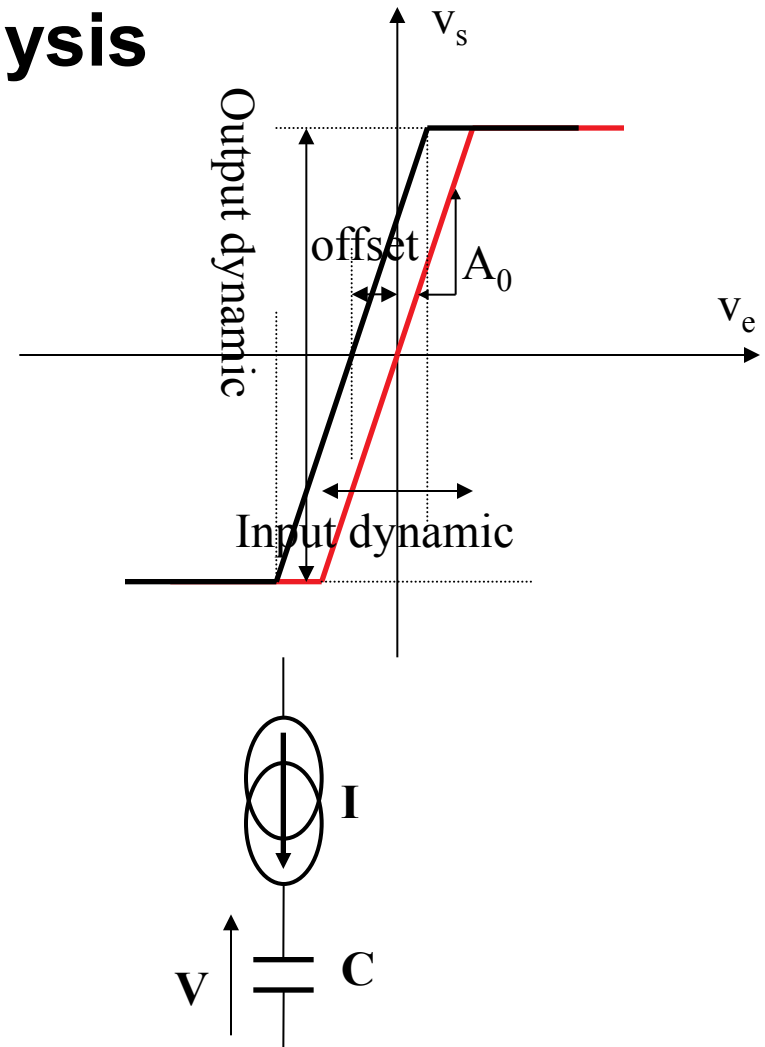


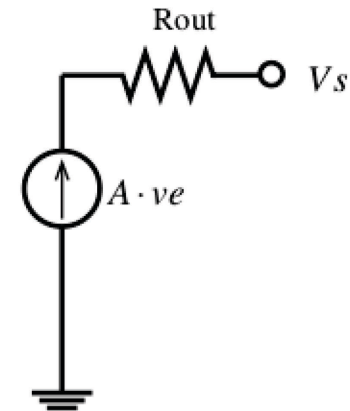
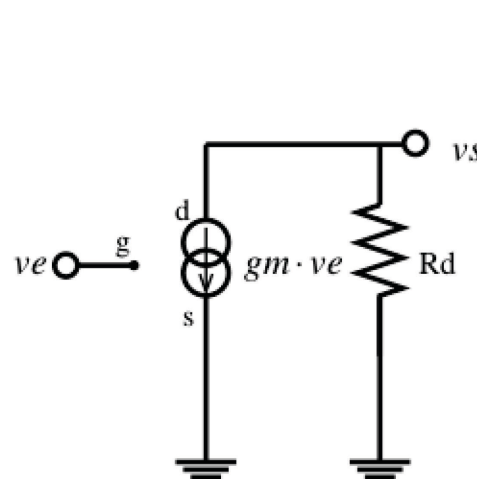
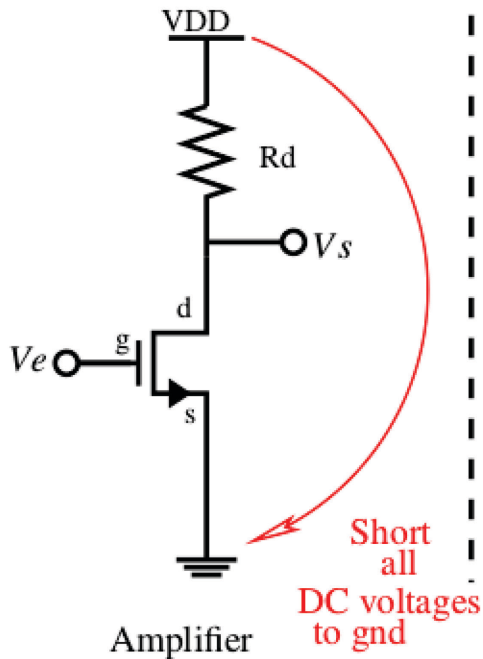
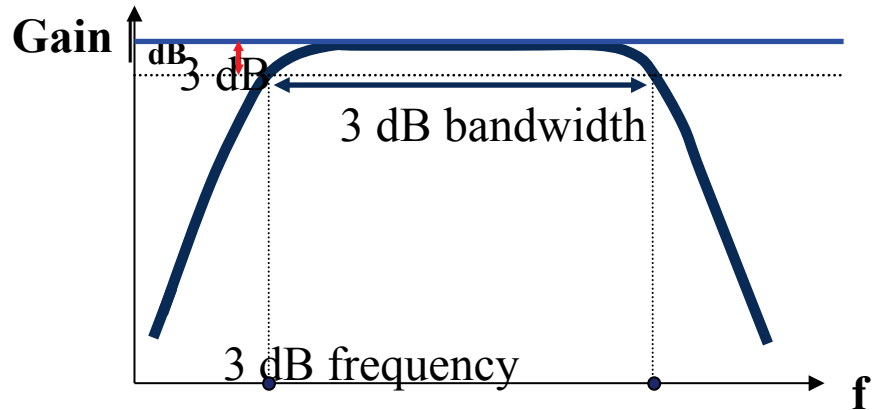
# Small signal

- Frequency response
- 3dB Bandwidth/Funity
- Output impedance



# Distortion

## Output signal is deformed

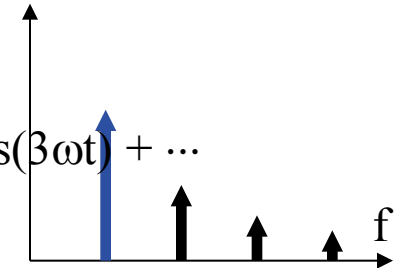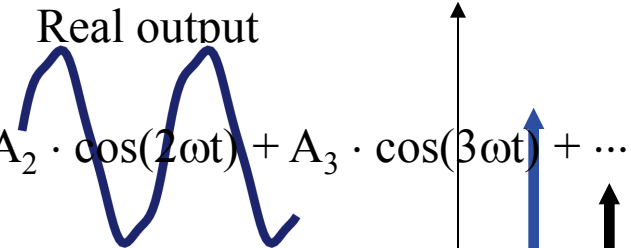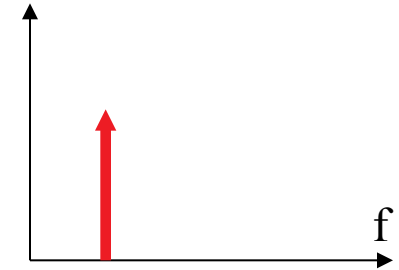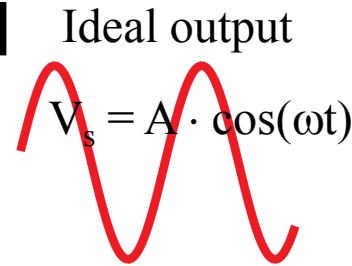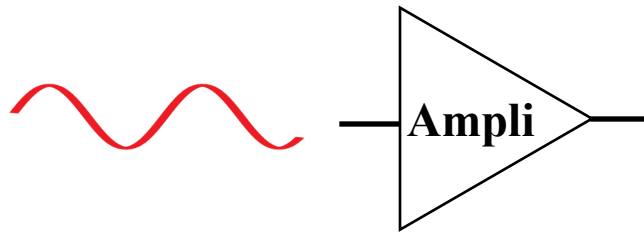

$A_2, A_3 \dots$  parasite amplification gains

### Distortion analysis


- Fourier analysis

### Distortion causes:

- Non linearity
- Saturation
- Slew-rate

# Distortion

## Intermodulation

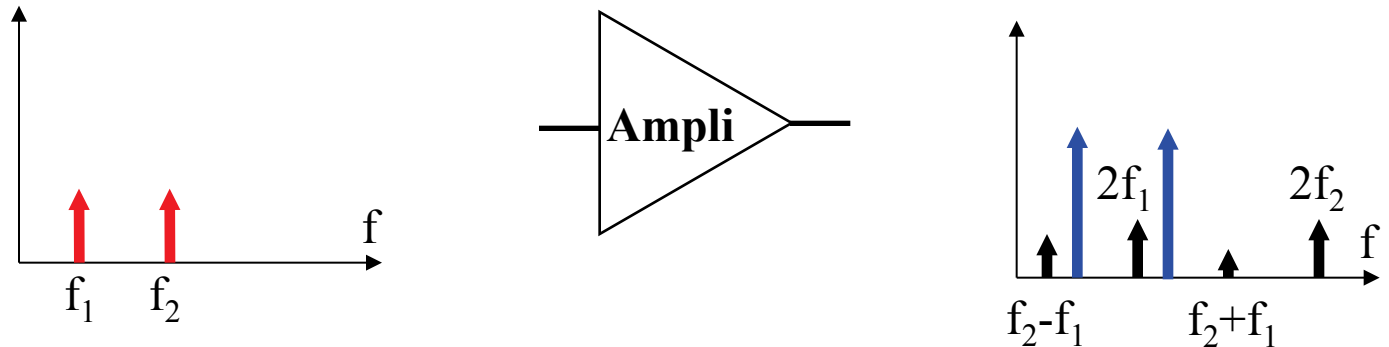


## Distortion ratio

$$V_s = A \cdot V_e + A_2 \cdot \cos(2\omega t) + A_3 \cdot \cos(3\omega t) + \dots$$

$$HD_2 = \left| \frac{A_2}{A} \right|$$

$$THD = \frac{\sqrt{A_2^2 + A_3^2 + \dots}}{|A|}$$

# Exercise: Harmonic decomposition

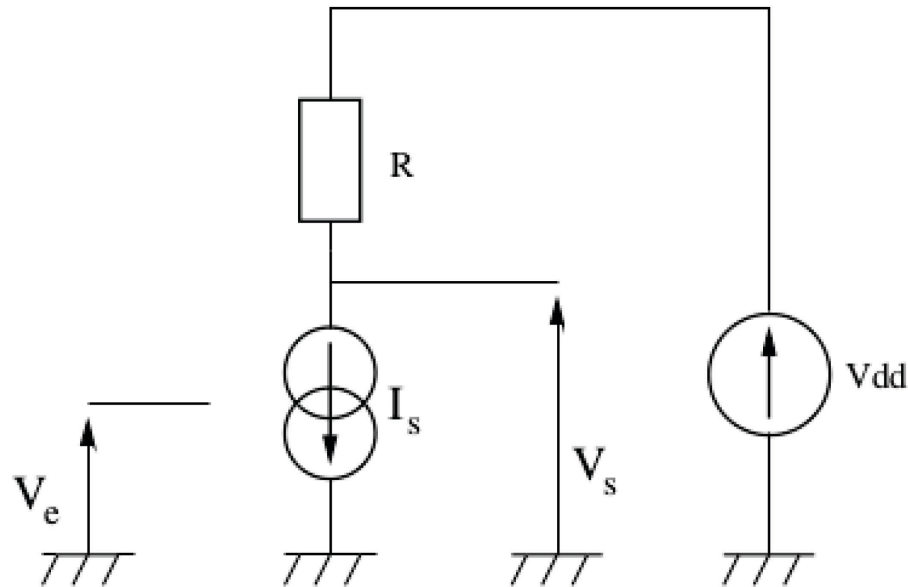

1. Calculate the harmonic decomposition of the output signal.
2. What is the THD of the amplifier?

# SNR, SNDR and Noise Figure

- **SNR : signal to noise ratio  $\Rightarrow$  quality of information transmission / parasites, noise**

$$SNR = \frac{\text{Signal power}}{\text{Noise power}} \Big|_{dB}$$



- **SNDR : signal to noise plus distortion ratio**

$$SNDR = \frac{\text{Signal power}}{\text{noise} + \text{distortion power}} \Big|_{dB}$$

- **Noise figure : ratio between SNR at the output and SNR at the input**



# Exercice: Gain, band. and distortion

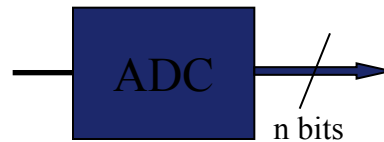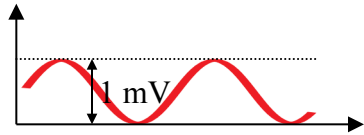

$n = 2$


$V_{\text{ref}}$	11
$3 V_{\text{ref}} / 4$	10
$V_{\text{ref}} / 2$	01
$V_{\text{ref}} / 4$	00
0	

$q = 1/2^8$

$n = 8, V_{\text{ref}} = 1$


1	11111111	1 V
	⋮	
$2 q$	00000001	
$q$	00000000	
0		

# Exercice: Gain, band. and distortion

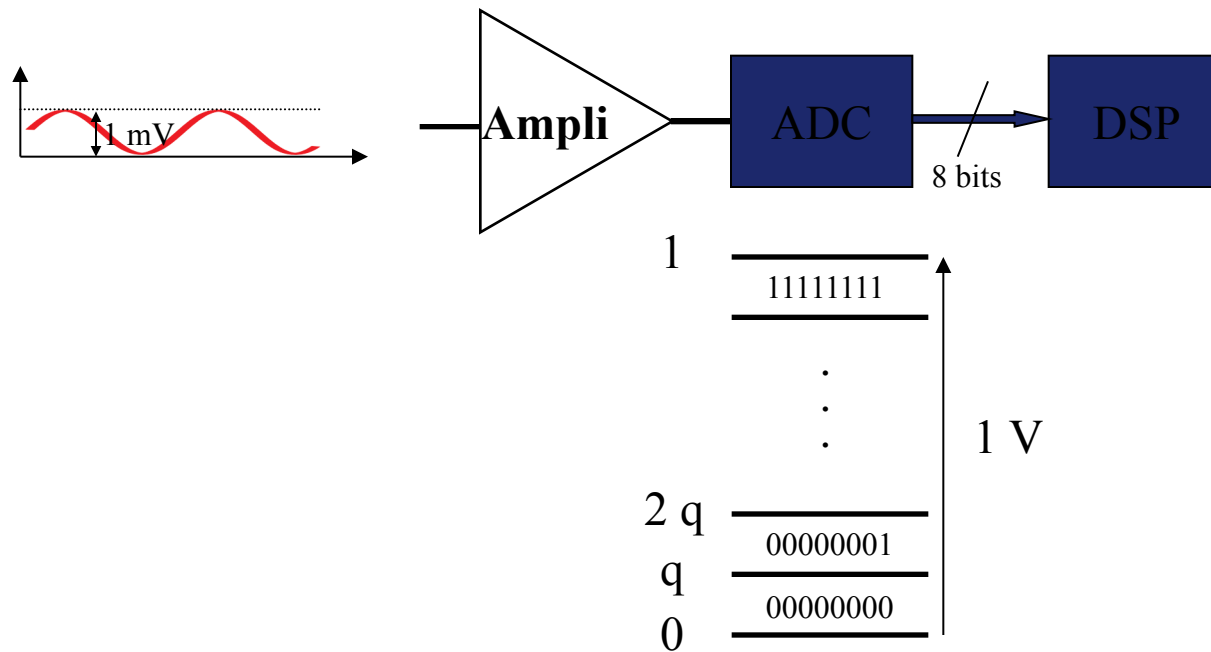


Gain et bandwidth ?

# Exercice: Gain, band. and distortion

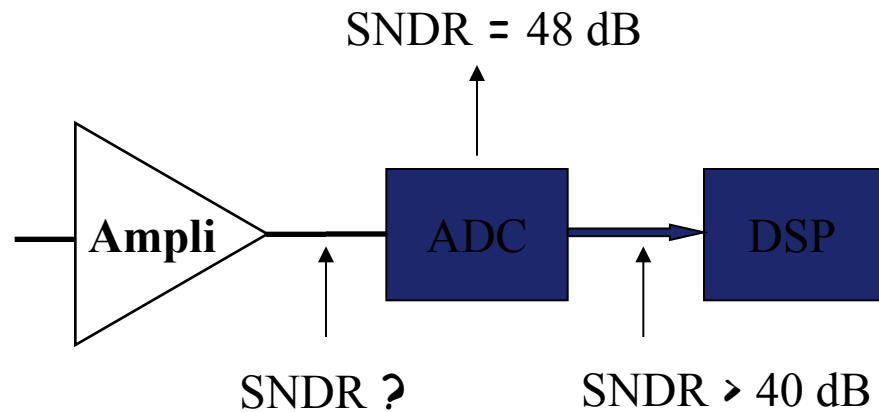

Maximum distortion?

# Differential amplifier

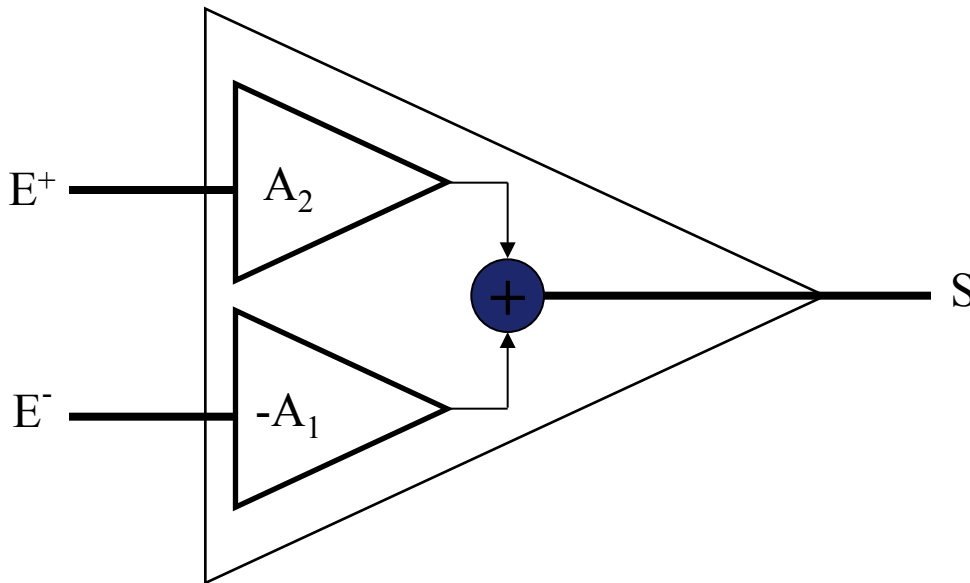

$$S = A_2 E^+ - A_1 E^-$$

$$E_d = E^+ - E^- \quad \text{et} \quad E_c = \frac{E^+ + E^-}{2}$$

$$A_d = \frac{A_1 + A_2}{2} \quad \text{et} \quad A_c = A_2 - A_1$$


$$S = A_d E_d + A_c E_c$$

Common mode rejection ratio

$$CMRR|_{dB} = 20 \log_{10} \left( \frac{A_d}{A_c} \right)$$

$$S = A_d \left( E_d + \frac{1}{CMRR} E_c \right)$$

# Operational amplifier

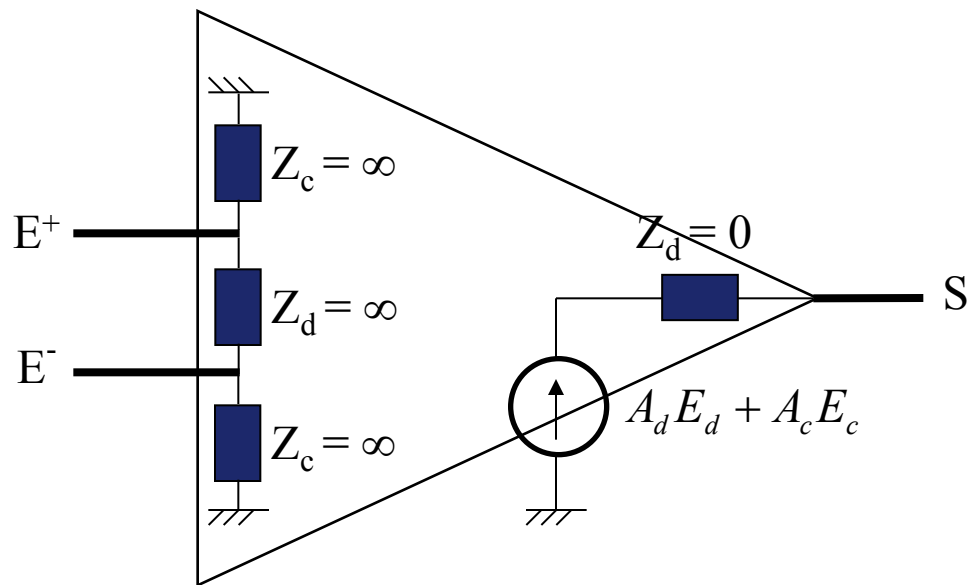

$$A_d = \infty \quad \text{and} \quad A_c = 0$$

$$A_d = \infty \quad \text{and} \quad \text{finite } S \Rightarrow E_d = \varepsilon = 0$$


# Characteristics

- Transition frequency :  $f_T$
- Gain margin GM
- Phase margin PM
- Gain bandwidth produ

$$PGB = A_0 \cdot f_c$$


$$A = A_0 \frac{1}{1 + j \frac{\omega}{\omega_c}}$$

$$f \gg f_c \Rightarrow |A| \cdot f = A_0 \cdot f_c$$

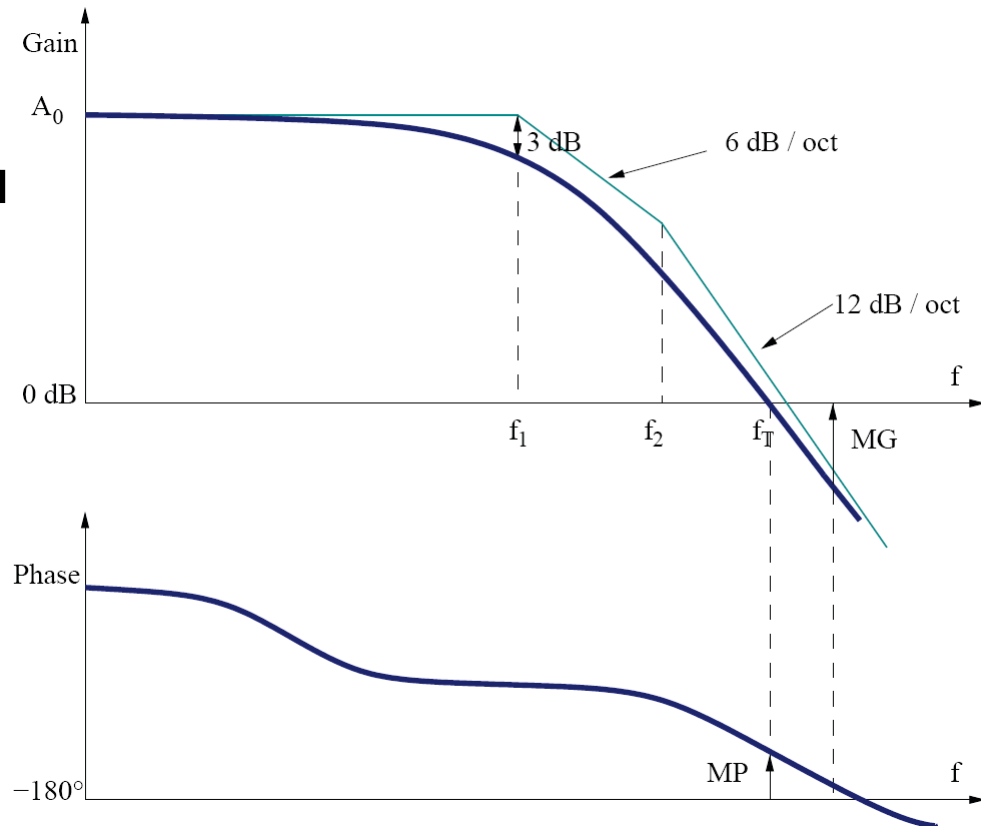

# Feedback

## Schema

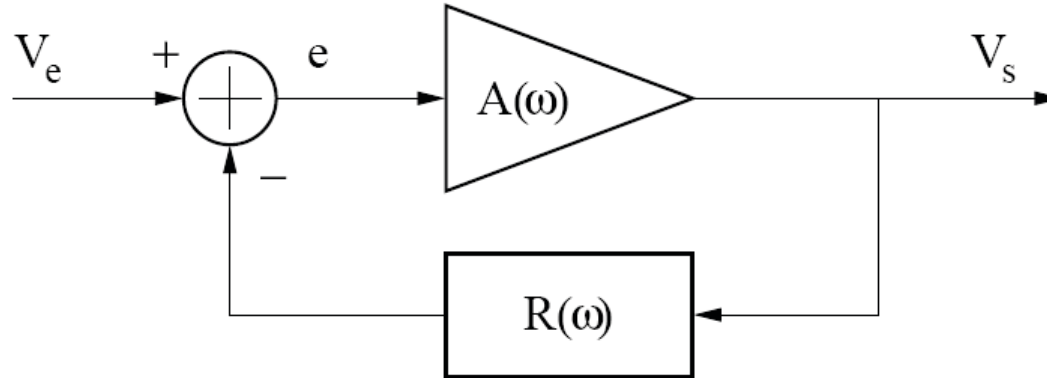

$$H(\omega) = \frac{A(\omega)}{1 + A(\omega)R(\omega)}$$

Feedback ratio

$$H(\omega) \approx \frac{1}{R(\omega)} \quad \text{si } A(\omega)R(\omega) \gg 1$$

# Feedback

**Advantages : Increase the bandwidth**

$$\text{If } R(\omega) = R \quad \text{and} \quad A(\omega) = \frac{A_0}{1 + j \frac{\omega}{\omega_c}}$$

$$H(\omega) = \frac{A_0}{1 + R \cdot A_0} \frac{1}{1 + j \frac{\omega}{\omega_c (1 + R \cdot A_0)}}$$



$$H_{BF0} = \frac{A_0}{1 + R \cdot A_0} \quad \omega_{BFC} = \omega_c (1 + R \cdot A_0)$$



# Feedback
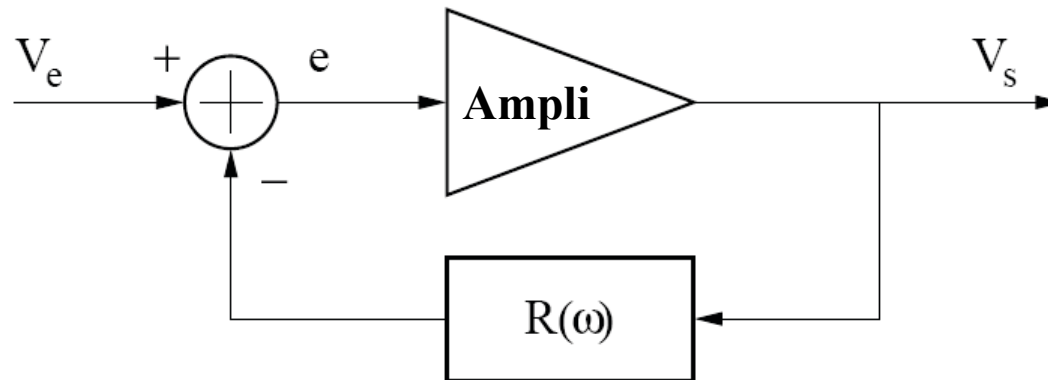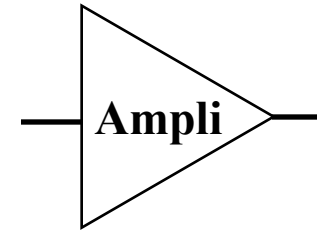
## Advantages : Distortion reduction



$$Y(\omega) = X(\omega) \cdot A(\omega) + u$$



$$(V_e(\omega) - R \cdot V_s(\omega))A(\omega) + u = V_s(\omega)$$

$$V_s(\omega) = \frac{A(\omega)}{1 + R \cdot A(\omega)} V_e(\omega) + \frac{1}{1 + R \cdot A(\omega)} u \ll u$$

# Exercice

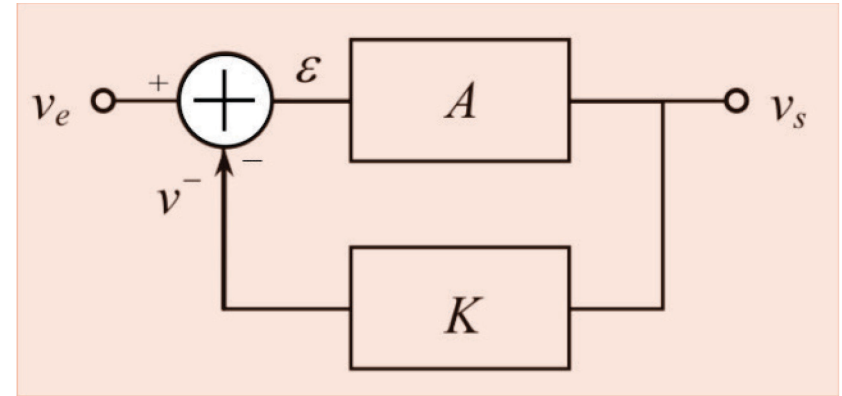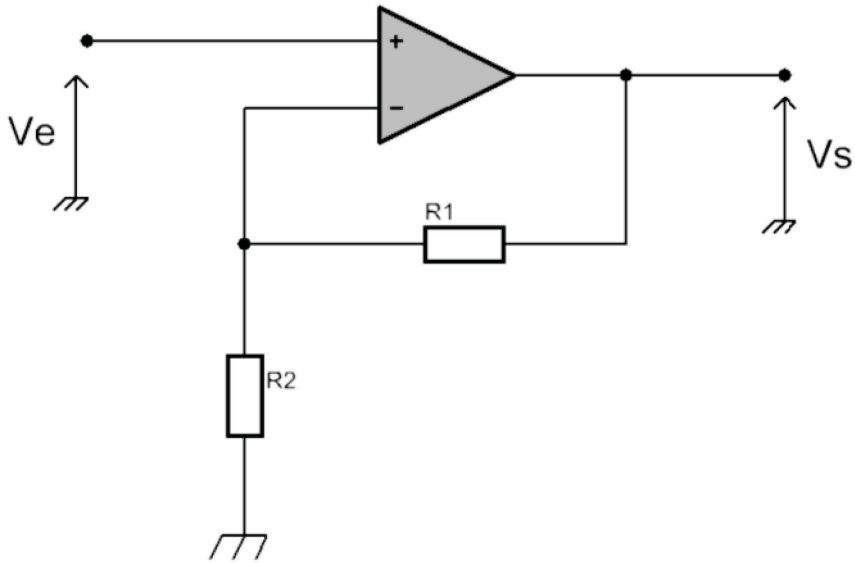

1. Calculate the transfer function  $H=V_s/V_e$  for an ideal OpAmp
2. What becomes  $H$  for a real OpAmp with a gain  $A$
3. Plot the Bode Diagram
4. How should we chose  $\tau_2$  to have a MP of  $\pi/4$ ?