

# Digital Systems exam (2 hours)

Renaud Pacalet - 2026-06-11

The text in black is the original one.

The text in red is examples of the expected correct answers. Only this text was expected, possibly in shorter form, nothing more.

The text in blue is extra comments about the expected correct answers.

Warning: the course changes frequently (content, vocabulary, examples...); some questions and answer proposals can thus be partly or completely out of scope. Warning: some questions can be answered in many different ways; the proposed answers are just examples and they are not exhaustive.

**The exam is closed book, closed notes, except one A4-sized, double sided, cheat sheet. Calculators are allowed but communicating devices are strictly forbidden.** Please number the different pages of your paper and indicate on each page your first and last names. You can write your answers in French or in English, as you wish. Precede your answers with the question's number. If some information or hypotheses are missing to answer a question, add them. If you consider a question as absurd and thus decide to not answer, explain why. If you do not have time to answer a question but know how to, briefly explain your ideas. Advice: quickly go through the document and answer the easy parts first. The first question is worth 4 points. The other questions are worth 2 points each. The problem is worth 10 points Use the provided VHDL cheat sheets at the end of this paper if you don't remember the syntax.

## 1. Questions

### 1.1. VHDL coding of a DFF with asynchronous reset

Bob has been asked to code in VHDL a D-flip-flop synchronized on rising edges of its clock and with active low **asynchronous** reset. The expected behaviour is represented by the waveforms of Figure 1 where `clk` is the clock, `rstn` is the reset, `d` is the data input and `q` is the data output.

 


Figure 1: The expected behaviour of the DFF

### 1.1.1. Bob's first coding attempt

Bob's first coding attempt is shown on Listing 1. Bob also coded a simulation environment for his DFF, that reproduces the behaviour of `clk`, `rstn` and `d` of Figure 1. He compiles with `ghdl`, without errors, and tries to simulate, but then `ghdl` raises an error:

```
$ ghdl -a --std=08 dff.vhd dff_sim.vhd
$ ghdl -r --std=08 dff_sim
dff.vhd:6:8:error: too many drivers for port "q"
      q:          out std_ulogic);
      ^
```

Can you explain this error? Where does it come from?

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity dff is
5      port(clk, rstn, d: in std_ulogic;
6           q:          out std_ulogic);
7  end entity dff;
8
9  architecture rtl of dff is
10 begin
11
12     reset: process(rstn)
13     begin
14         if rstn = '0' then
15             q <= '0';
16         end if;
17     end process;
18
19     clock: process(clk)
20     begin
21         if rising_edge(clk) then
22             q <= d;
23         end if;
24     end process;
25
26 end architecture rtl;
```

Listing 1: Bob's first coding attempt

The `q` port is of type `std_ulogic`, which is unresolved, so `q` cannot be driven by two or more processes, as Bob tried to do.

Only signals of resolved types, like `std_logic`, can be driven by several processes. These types have an associated resolution function that is called by the simulator to compute the resulting value from the different values that the different processes drive.

### 1.1.2. Bob's second coding attempt

Bob asks how to fix this to the new AI of the company, which suggests to replace type `std_ulogic` with type `std_logic`. Bob edits his two VHDL source files, re-compiles and simulates. Unfortunately, the waveforms (see Figure 2) are not what Bob was expecting

 


Figure 2: The behaviour of Bob's second attempt

Can you explain this behaviour? Where does it come from? What do you think of the AI's suggestion?

As the q port is now of type `std_logic`, which is resolved, there is no error, even if there are two driving processes. On the first value change to '0' of `rstn` the first process (`reset`) starts driving q to value '0', and this driving never stops until the end of the simulation, even when `rstn` changes again. As long as the two processes agree on the driving value everything is fine, but when they disagree, and one drives '0' while the other drives '1', the resolution function outputs 'X' (unknown). The AI's suggestion is indeed a way to fix the error message that Bob reported, but it does not help implementing the expected behaviour.

### 1.1.3. Bob's third coding attempt

Bob decides to ask Mary, who seems to be better at VHDL coding than the new AI. Mary recommends to use type `std_ulogic` but only one process instead of two. Bob reworks his code as shown on Listing 2. He compiles and simulates. The waveforms he obtains are shown on Figure 3.

```

1  architecture rtl3 of dff is
2  begin
3
4      process(clk)
5      begin
6          if rstn = '0' then
7              q <= '0';
8          elsif rising_edge(clk) then
9              q <= d;
10         end if;
11     end process;
12
13 end architecture rtl3;
```

Listing 2: Bob's third coding attempt

 


Figure 3: The behaviour of Bob's second attempt

Bob is very happy because this time everything looks fine, until he shows that to Jane, his manager, who immediately spots a difference with the expected behaviour. On Figure 3 the expected behaviour of output `q` is represented as a dashed line and the difference is circled.

Can you explain this behaviour? Where does it come from?

The reset is supposedly **asynchronous** but as Bob forgot to add it in the sensitivity list of his process, it is taken into account only on value changes of `clk` (rising **and** falling edges), which is not the expected behaviour. This is why the first falling edge of `rstn` does not have an immediate effect on `q`; it is only on the following value change of `clk` that `q` is assigned '0'.

#### 1.1.4. Your coding attempt

Bob is a bit desperate and decides to ask your help, because, even if you are very busy, he knows that you will solve this in a matter of minutes. Write down a correct architecture for the DFF, explain the differences with Bob's third attempt.

Simply adding the reset `rstn` to the sensitivity list of the process solves the issue:

```
...
process(clk, rstn)
...

```

## 1.2. Range of integer variables and signals

Why is it preferable to specify the range of variables and signals of integer type?

First because a synthesizer uses this information to instantiate the exact bit number: an integer type object without range constraint synthesizes in a 32 bits object. Second because the simulator dynamically checks the constraint and this is an interesting debugging feature.

## 1.3. State machines

What are the differences between a Mealy and a Moore state machine? What are their advantages and drawbacks?

In a Mealy machine the outputs depend on the current state and on the inputs. In a Moore state machine the outputs depend only on the current state.

In some cases, for the same functional specification, a Mealy state machine requires fewer states than its Moore counterpart, which may be considered as an advantage, especially when it leads to a smaller and less power consuming design.

The main drawback of Mealy machines is their combinational paths between the primary inputs and the primary outputs. When connecting Mealy machines in a chain, the critical path increases while it doesn't with Moore machines.

If the outputs of a state machine are control signals of a datapath (a frequent situation) they may be connected to many logic gates (e.g., multiplexers), and consequently they can be heavily loaded (capacitive). In such situations they can be slow changing signals, which increases the critical path of the whole design. In such cases Moore could be preferred.

Note: when it is feasible, computing these control signals one clock cycle ahead and sampling them in registers can be an interesting solution. It reduces the impact on the critical path to its minimum and it makes Moore and Mealy equally usable.

## 1.4. Logic synthesis

In your opinion, how many bits of register will be inferred when synthesizing the VHDL code of Listing 3? Draw a schematic of the synthesis result. Could we obtain the same behaviour with less registers?

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity bsk is
5      port(clk: in std_ulogic;
6            din: in std_ulogic_vector(11 downto 0);
7            dout: out std_ulogic_vector(11 downto 0));
8  end entity bsk;
9
10 architecture rtl of bsk is
11     signal a, b: std_ulogic_vector(11 downto 0);
12 begin
13     process(clk)
14     begin
15         if rising_edge(clk) then
16             a <= din;
17             b <= a;
18             dout <= a or b;
19         end if;
20     end process;
21 end architecture rtl;
```

Listing 3: Synthesizable model

36 bits of register will be inferred.

The 2 signals `a`, `b` and the output port `dout` are assigned on rising edges of `clk`. So, one register is inferred by the synthesizer for each of them. They are 12 bits wide, so  $3 \times 12 = 36$  bits of register are inferred.

The schematic is shown on Figure 4.

 


Figure 4: Schematic of the synthesis result

There is no way to obtain the **exact** same timing **and** functional behaviour with less registers.

But if the goal is only to compute the bitwise OR of two consecutive values of `din`, and the timing of the output is not relevant, a 12-bits register could suffice, as shown on Figure 5 and Listing 4.

 


Figure 5: Schematic of the synthesis result of the optimized version

```

1 architecture rtl2 of bsk is
2   signal a: std_ulogic_vector(11 downto 0);
3 begin
4   process(clk)
5     begin
6       if rising_edge(clk) then
7         a <= din;
8       end if;
9     end process;
10    dout <= a or din;
11 end architecture rtl2;

```

Listing 4: Optimized synthesizable model

Let us denote  $x[n]$  the value of signal  $x$  at rising edge number  $n$  of `clk`, and `reg_x` the register with output  $x$ . One could think that there is a kind of redundancy between the three 12-bits registers but they correspond to different times: during the clock period between rising edges  $n$  and  $n+1$ , `reg_a` stores  $din[n]$ , `reg_b` stores  $din[n-1]$ , and `reg_dout` stores  $din[n-2]$  OR  $din[n-3]$ . Removing `reg_a`, for instance, by assigning

directly `b <= din`, would change the timing behaviour because during the clock period between rising edges `n` and `n+1`, the value of `dout` would now be `din[n-1] OR din[n-2]` instead of `din[n-2] OR din[n-3]`.

With the “optimized” version, the value of `dout` during the clock period between rising edges `n` and `n+1` is `din[n] OR din[n-1]`.

## 2. Problem: design and VHDL coding of a pipelined generic parity calculator

The goal of this problem is to design and code in synthesizable VHDL 2008 a generic, pipelined, parity calculator: `par`. It takes a multi-bits input `din` and computes its one-bit parity, that is, the exclusive OR of all bits of `din`. If `din` contains an even number of bits equal to '1', its parity is '0', else it is '1'. The bit width of `din` is greater or equal 2 and is a power of 2 (2, 4, 8,...)

`par` is generic; it has a generic parameter `n` of type `positive` which is the logarithm in base 2 of the bit width of the `din` input: if `n=1`, `din` is a two-bits vector, if `n=2`, `din` is a four-bits vector, ..., if `n=10`, `din` is a 1024-bits vector, ... Table 1 describes the interface of `par`.

Name	Direction	Bit width	Description
<code>clk</code>	input	1	clock
<code>srstn</code>	input	1	active low synchronous reset
<code>load</code>	input	1	load control signal
<code>din</code>	input	$2^n$	data input
<code>dso</code>	output	1	'1' when output valid
<code>do</code>	output	1	parity output

Table 1: Interface of `par`

As we need very high performance `par` is pipe-lined: the parity is computed in `n` successive clock cycles. When the `load` control signal is equal to '1' on a rising edge of the clock `clk`, `din` is stored in a  $2^n$ -bits input register. During the following clock cycle the content of the input register is processed: each pair of bits is XOR-ed and the result is stored in a second  $2^{n-1}$  bits register; during the following clock cycle each pair of bits of this first intermediate result is XOR-ed and the result is stored in another  $2^{n-2}$  bits register; and so on until there is only one remaining result bit, which is stored in a last one-bit register. The `do` output is the output of this last one-bit register.

Thanks to this pipelined architecture a new input can be submitted at each clock cycle. But as there is not always a new input to process the `load` control signal indicates at which clock cycles new inputs are submitted.

The `dso` output is set to '1' by `par` during one clock cycle when a valid parity result is available at the `do` output. This way the environment can sample `do` on each rising edge of `clk` where `dso='1'`. Note: if `load='1'` at rising edge number `x` of `clk`, then `par` sets `dso` to '1' during the clock period between rising edges `x + n` and `x + n + 1`, such that `dso='1'` on rising edge `x + n + 1`.

The active low **synchronous** reset `srstn` is used to reinitialize `par`: when `srstn='0'` on a rising edge of `clk`, all bits of the internal registers are set to '0', and any ongoing computation is aborted.

## 2.1. Design of block and state diagrams

Draw a block diagram of `par` with `n=3` using the symbols represented on Figure 6. Clearly identify the registers, give their size in bits, name them and explain what their role is.

If you use state machines represent them as “other synchronous elements” in your block diagram, with named inputs and outputs. Draw their state diagrams, explain whether they are Moore or Mealy state machines, and provide a description of their role.

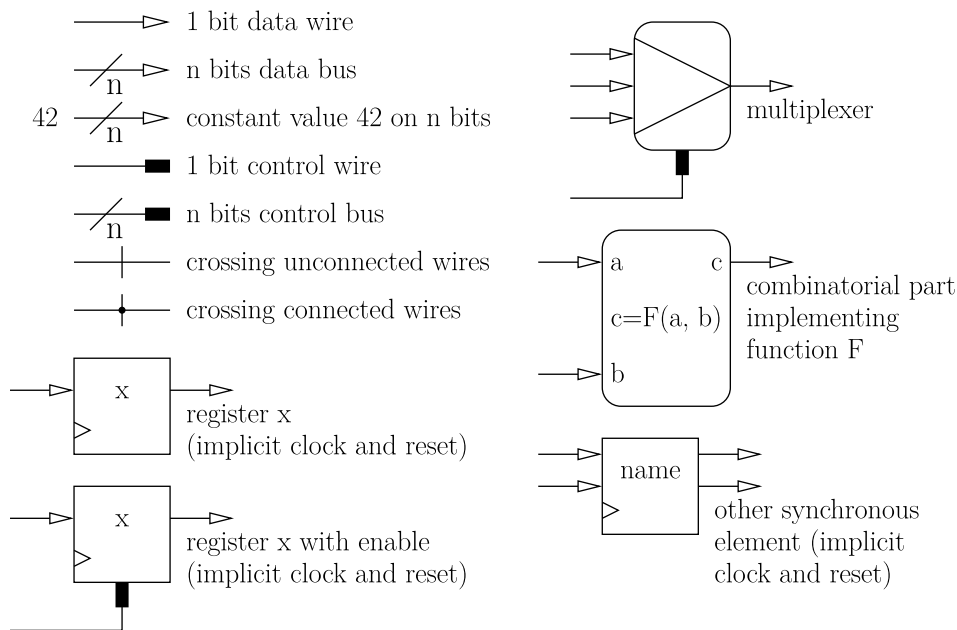


Figure 6: Symbols to design block diagrams

The block diagram of `par3` is shown on Figure 7 where the synchronous reset has been omitted for better readability. The `b = xh(a)` combinational block outputs the XOR of the two halves of its input bus `a`, which size must of course be even. The `dso` output is handled with the simple 4-stages `rd` shift register which serial input is `load`. The other registers are the 4 data registers of the specification: `r3` is the 8-bits input register that stores `din`, `r2` is the 4-bits first intermediate register, `r1` is the 2-bits next intermediate register, and `r0` is the 1-bit last register, which output is `do`.

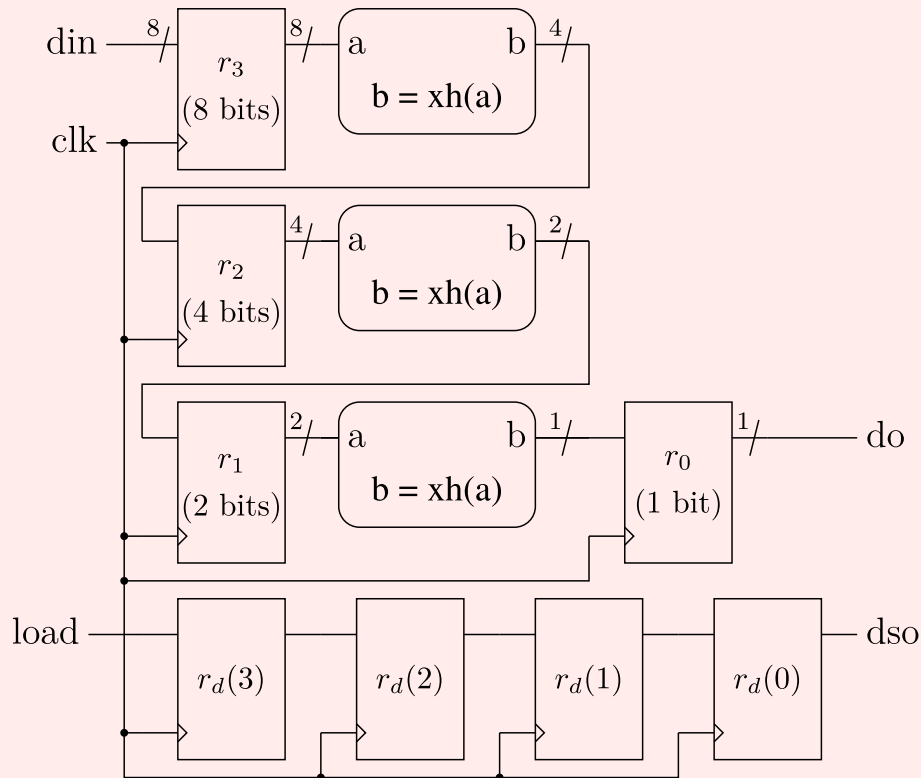


Figure 7: Block diagram of `par3`

## 2.2. VHDL coding for `n=3`

As an intermediate step, we consider `par3`, a non-generic version of `par` which `din` input is 8 bits wide. Code `par3` (entity and architecture) in synthesizable VHDL 2008. Do not use sub-designs and entity instantiations: code everything in the `par3` architecture. Add comments to explain non-obvious parts of your code.

The synthesizable VHDL 2008 model of `par3` is shown on Listing 5. The  $b = xh(a)$  combinatorial block of Figure 7 is implemented as the `xh` helper function.

Note how the function uses constants `size`, `lv` (a copy of the input parameter with known bounds), and `res`, to not depend on the actual bounds of the input parameter and to control the bounds of the returned vector.

The other parts are straightforward VHDL translation of the block diagram.

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity par3 is
5     port(clk, srstn, load: in std_ulogic;
6           din: in std_ulogic_vector(7 downto 0);
7           do, dso: out std_ulogic);
8 end entity par3;
9
10 architecture rtl of par3 is
11
12     signal rd: std_ulogic_vector(3 downto 0);
13     signal r0: std_ulogic; -- could also be a 1-bit vector
14     signal r1: std_ulogic_vector(1 downto 0);
15     signal r2: std_ulogic_vector(3 downto 0);
16     signal r3: std_ulogic_vector(7 downto 0);
17
18     function xh(v: std_ulogic_vector) return std_ulogic_vector is
19         constant size: natural := v'length;
20         constant lv: std_ulogic_vector(size - 1 downto 0) := v;
21         constant res: std_ulogic_vector(size / 2 - 1 downto 0) :=
22             lv(size - 1 downto size / 2) xor lv(size / 2 - 1 downto 0);
23     begin
24         return res;
25     end function xh;
26
27 begin
28
29     process(clk)
30     begin
31         if rising_edge(clk) then
32             if srstn = '0' then
33                 rd <= (others => '0');
34                 r0 <= '0'; -- scalar, not vector
35                 r1 <= (others => '0');
36                 r2 <= (others => '0');
37                 r3 <= (others => '0');
38             else
39                 rd <= load & rd(3 downto 1);
40                 r0 <= xh(r1)(0); -- scalar, not vector
41                 r1 <= xh(r2);
42                 r2 <= xh(r3);
43                 r3 <= din;
44             end if;
45         end if;
46     end process;
47
48     do <= r0; -- scalar, not vector
49     dso <= rd(0);
50
51 end architecture rtl;

```

Listing 5: VHDL model of par3

## 2.3. VHDL coding for any value of n

Code par (entity and architecture) in synthesizable VHDL 2008, for **any** value of generic parameter n. Do not use sub-designs and entity instantiations: code everything in the par architecture. Add comments to explain non-obvious parts of your code.

The synthesizable VHDL 2008 model of `par` is shown on Listing 6. It is based on the same principles as `par3`, with data registers  $r_n, \dots, r_1, r_0$ , where  $r_n$  is the input register and  $r_0$  is the output register. The main difference is that the number of data registers ( $n + 1$ ) depends on the `n` generic parameter. They can thus not be declared individually.

Instead, we declare the array type `r_t`, with  $n + 1$  elements indexed from 0 to  $n$  where each element is a  $2^n$ -bits vector, that is, the size of the input register, the largest of all. Then, we declare `r`, a signal of this type, to represent the outputs of all the data registers: `r(n)` is the output of  $r_n$ , ..., and `r(0)` is the output of  $r_0$ .

Except for the input register,  $2^n$ -bits is larger than needed but, as we use only the least significant bits, the synthesizer/optimizer will simply eliminate the useless register bits.

The data passing between the data registers is implemented as a for loop where the index `i` is that of the destination register in array `r`.

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity par is
5     generic(n: positive);
6     port(clk, srstn, load: in std_ulogic;
7         din: in std_ulogic_vector(2**n - 1 downto 0);
8         do, dso: out std_ulogic);
9 end entity par;
10
11 architecture rtl of par is
12
13     function xh(v: std_ulogic_vector) return std_ulogic_vector is
14         constant size: natural := v'length;
15         constant lv: std_ulogic_vector(size - 1 downto 0) := v;
16         constant res: std_ulogic_vector(size / 2 - 1 downto 0) :=
17             lv(size - 1 downto size / 2) xor lv(size / 2 - 1 downto 0);
18     begin
19         return res;
20     end function xh;
21
22     type r_t is array(0 to n) of std_ulogic_vector(2**n - 1 downto 0);
23     signal r: r_t;
24     signal d: std_ulogic_vector(n downto 0);
25
26     begin
27
28         process(clk)
29         begin
30             if rising_edge(clk) then
31                 if srstn = '0' then
32                     r <= (others => '0');
33                     d <= (others => '0');
34                 else
35                     for i in 0 to n - 1 loop
36                         r(i)(2**i - 1 downto 0) <= xh(r(i + 1)(2**(i + 1) - 1 downto 0));
37                     end loop;
38                     r(n) <= din;
39                     d <= load & d(n downto 1);
40                 end if;
41             end if;
42         end process;
43
44         do <= r(0)(0); -- r(0) is a vector, not a scalar
45         dso <= d(0);
46
47     end architecture rtl;

```

Listing 6: VHDL model of par

We can also declare only the necessary register bits, that is,  $2^n + 2^{n-1} + \dots + 2 + 1 = 2^{n+1} - 1$  bits:

```
signal r: std_ulogic_vector(2**(n+1) - 2 downto 0);
```

This is sufficient to implement all data registers as shown on Figure 8.

 


Figure 8: Registers mapping of the alternate model of par

From Figure 8 and some basic arithmetics we immediately see that  $r_i$  (with  $0 \leq i \leq n$ ) is slice  $2^{i+1} - 2 \dots 2^i - 1$  of  $r$ . So, we map data register  $r_i$  to  $r(2^{i+1} - 2$  downto  $2^i - 1)$ . The input register  $r_n$ , for instance, is mapped to  $r(2^{n+1} - 2$  downto  $2^n - 1)$ , and the output register  $r_0$  is mapped to  $r(0)$ . This does not rely on the synthesizer/optimizer to remove the unused register bits, but the for loop is a bit more complicated as Listing 7 shows.

```

1  architecture rtl2 of par is
2
3      function xh(v: std_ulogic_vector) return std_ulogic_vector is
4          constant size: natural := v'length;
5          constant lv: std_ulogic_vector(size - 1 downto 0) := v;
6          constant res: std_ulogic_vector(size / 2 - 1 downto 0) :=
7              lv(size - 1 downto size / 2) xor lv(size / 2 - 1 downto 0);
8      begin
9          return res;
10     end function xh;
11
12     signal r: std_ulogic_vector(2**(n + 1) - 2 downto 0);
13     signal d: std_ulogic_vector(n downto 0);
14
15 begin
16
17     process(clk)
18     begin
19         if rising_edge(clk) then
20             if srstn = '0' then
21                 r <= (others => '0');
22                 d <= (others => '0');
23             else
24                 for i in 0 to n - 1 loop
25                     r(2**(i + 1) - 2 downto 2**i - 1) <=
26                         xh(r(2**(i + 2) - 2 downto 2**(i + 1) - 1));
27                 end loop;
28                 r(2**(n + 1) - 2 downto 2**n - 1) <= din;
29                 d <= load & d(n downto 1);
30             end if;
31         end if;
32     end process;
33
34     do <= r(0);
35     dso <= d(0);
36
37 end architecture rtl2;

```


Listing 7: Alternate VHDL model of par

## 2.4. Power optimization

Assume that, after a number of parity computations, there are no more inputs to submit to `par` for some (long) time. Will your design still consume power, even if there is nothing to compute? If no explain why. Else suggest ways to reduce this useless power consumption; do not code in VHDL, just explain what should be done to save power.

The design will still consume power if the `din` input changes, even if `load` remains zero. Indeed, the parity will still be computed. It is only `dso` that will remain zero to indicate that these parity outputs shall be ignored. But the toggling of all the internal wires will consume power. To prevent this we could sample `din` in the input register only if `load = '1'`. The power would then decrease because once all internal registers converged to their final value there would be no more wire toggling.

 However, if the clock is still active, there will still be its own power consumption, unless a power saving mode is implemented and the clock generator stops the clock. But this last technique does not depend on our design.



# VHDL QUICK REFERENCE CARD

Revision 2.2

{}	Grouping	[]	Optional
{}	Repeated		Alternative
<b></b>	As is	CAPS	User Identifier
<i></i>	VHDL-1993		

## 1. LIBRARY UNITS

```

[use_clause]
entity ID is
  [generic {ID : TYPEID [= expr];}]
  [port {ID : in | out | inout TYPEID [= expr];}]
  [(declaration)]
begin
  {parallel_statement}
end [entity] ENTITYID;

[use_clause]
architecture ID of ENTITYID is
  [(declaration)]
begin
  [{parallel_statement}]
end [architecture] ARCHID;

[use_clause]
package ID is
  [(declaration)]
end [package] PKGID;

[use_clause]
package body ID is
  [(declaration)]
end [package body] PKGID;

[use_clause]
configuration ID of ENTITYID is
  for ARCHID
    [block_config | comp_config]
  end for;
end [configuration] CONFID;

use_clause ::=
  library ID;
  [use LIBID.PKGID; all | DECLID;]
block_config ::=

```

## 2. DECLARATIONS

### 2.1. TYPE DECLARATIONS

```

for LABELID
  [block_config | comp_config]
end for;

comp_config ::=
  for all | LABELID : COMPID
    (use entity [LIBID.]ENTITYID ([ ARCHID ])
     [generic map ({GENID => expr ,})]
     port map ({PORTID => SIGID | expr ,}));
  [for ARCHID
    [block_config | comp_config]
  end for;]
end for;]
(use configuration [LIBID.]CONFID
 port map ({PORTID => SIGID | expr ,}));
end for;

```

### 2.2. OTHER DECLARATIONS

```

type ID is ( {ID ,} );
type ID is range number downto | to number;
type ID is array ( {range | TYPEID ,} ) of TYPEID;
type ID is record
  {ID : TYPEID; }
end record;
type ID is access TYPEID;
type ID is file of TYPEID;
subtype ID is SCALARTYPEID range range;
subtype ID is ARRAYTYPEID( {range ,} );
subtype ID is RESOLVCTID TYPEID;

range ::=
  (integer | ENUMID to | downto integer | ENUMID) |
  (OBJID [reverse_]range) | (TYPEID range <=>)

```

### 2.2. OTHER DECLARATIONS

```

constant ID : TYPEID := expr;
[shared] variable ID : TYPEID [= expr];
signal ID : TYPEID [= expr];

file ID : TYPEID ( {s in | out string ,} )
  (open read_mode | write_mode |
  append_mode is string);
alias ID : TYPEID is OBJID;
attribute ID : TYPEID;
attribute ATTRID of OBJID | others | all : class is expr;
class ::=
  entity | architecture | configuration |
  procedure | function | package | type |
  subtype | constant | signal | variable |
  component | label

```

## 3. EXPRESSIONS

```

component ID [ {s} ]
  [generic {ID : TYPEID [= expr];}]
  [port {ID : in | out | inout TYPEID [= expr];}]
end component [COMPID];

[impure | pure] function ID
  [( {constant | variable | signal | file ID :
  [in] TYPEID [= expr];}]
  return TYPEID [ {s}
begin
  {sequential_statement}
end [function] ID];
procedure ID[( {constant | variable | signal ID :
  in | out | inout TYPEID [= expr];}]
[is begin
  {sequential_statement}
end [procedure] ID];

for LABELID | others | all : COMPID use
  (entity [LIBID.]ENTITYID ([ ARCHID ]) |
  (configuration [LIBID.]CONFID)
  [generic map ({GENID => expr ,})]
  port map ({PORTID => SIGID | expr ,}));

```

### 3.1. OPERATORS, INCREASING PRECEDENCE

```

expression ::=
  (relation and relation) | (relation nand relation) |
  (relation or relation) | (relation nor relation) |
  (relation xor relation) | (relation xnor relation)
relation ::= sheqpr [relop sheqpr]
sheqpr ::= sexpr [shop sexpr]
sexpr ::= [+|-] term {addop term}
term ::= factor {mulop factor}
factor ::=
  (prim ["" prim]) | (abs prim) | (not prim)
prim ::=
  literal | OBJID | OBJID.ATTRID | OBJID(expr ,)
  | OBJID(range) | ((choice { [choice] => } expr ,)
  | FCTID({PARID => } expr ,) | TYPEID(expr) |
  TYPEID(expr) | new TYPEID[(expr)] | (expr)
choice ::= sexpr | range | RECFID | others

```

### 3.1. OPERATORS, INCREASING PRECEDENCE

```

logop      and | or | xor | nand | nor | xnor
relop     = | /= | < | <= | > | >=
shop      s// | sr/ | sla | sra | rol | ror
addop     + | - | * | / | mod | rem
mulop     * | / | mod | rem
miscop    ** | abs | not

```

1995-2000 Qualis Design Corporation. Permission to reproduce and distribute strictly verbatim copies of this document in whole is hereby granted.

See reverse side for additional information.

#### 4. SEQUENTIAL STATEMENTS

```

wait (on {SIGID,}) [until expr] [for time];
assert expr
  [report string]
  [severity note | warning | error | failure];
report string
  [severity note | warning | error | failure];
SIGID <= [transport] | [[reject TIME] inertial]
  {expr [after time],};
VARID := expr;
PROCEDUREID([PARID =>] expr,);
[LABEL:] if expr then
  {sequential_statement}
[elseif expr
  {sequential_statement}]
[else
  {sequential_statement}]
end if [LABEL:];
[LABEL:] case expr is
  {when choice [{choice}] =>
  {sequential_statement}}
end case [LABEL:];
[LABEL:] while expr loop
  {sequential_statement}
end loop [LABEL:];
[LABEL:] for ID in range loop
  {sequential_statement}
end loop [LABEL:];
next [LOOPLBL] [when expr];
exit [LOOPLBL] [when expr];
return [expression];
null;

```

#### 5. PARALLEL STATEMENTS

```

LABEL: block [is]
  [generic ({ID : TYPEID,}):]
  [port ({ID : in | out | inout TYPEID },):]
  [port map ({PORTID =>} SIGID | expr,):]
  [(declaration)]
begin
  [[parallel_statement]]
end block [LABEL:];
[LABEL:] [postponed] process [( {SIGID, })]
  [(declaration)]
begin
  [[sequential_statement]]
end [postponed] process [LABEL:];
[LBL:] [postponed] PROCID([PARID =>] expr,);

```

```

[LABEL:] [postponed] assert expr
  [report string]
  [severity note | warning | error | failure];
[LABEL:] [postponed] SIGID <=
  [transport] | [[reject TIME] inertial]
  [{expr [after TIME,]} | unaffected;
  {expr [after TIME,]} | unaffected];
[LABEL:] [postponed] with expr select
  SIGID <= [transport] | [[reject TIME] inertial]
  {expr [after TIME,]} | unaffected
  when choice [{choice]};

```

#### 6. PREDEFINED ATTRIBUTES

```

LABEL: COMPID
  [[generic map ( {GENID => expr, })]
  port map ( {PORTID =>} SIGID | expr, )];
LABEL: entity [LIBID,] ENTITYID ([ARCHID])
  [[generic map ( {GENID => expr, })]
  port map ( {PORTID =>} SIGID | expr, )];
LABEL: configuration [LIBID,] CONFIGID
  [[generic map ( {GENID => expr, })]
  port map ( {PORTID =>} SIGID | expr, )];
LABEL: if expr generate
  [[parallel_statement]]
end generate [LABEL:];
LABEL: for ID in range generate
  [[parallel_statement]]
end generate [LABEL:];

```

TYPEID'base	Base type
TYPEID'left	Left bound value
TYPEID'right	Right-bound value
TYPEID'high	Upper-bound value
TYPEID'low	Lower-bound value
TYPEID'pos(expr)	Position within type
TYPEID'val(expr)	Value at position
TYPEID'succ(expr)	Next value in order
TYPEID'pred(expr)	Previous value in order
TYPEID'leftof(expr)	Value to the left in order
TYPEID'rightof(expr)	Value to the right in order
TYPEID'ascending	Ascending type predicate
TYPEID'image(expr)	String image of value
TYPEID'value(string)	Value of string image
ARYID'left(expr)	Left-bound of [nth] index
ARYID'right(expr)	Right-bound of [nth] index
ARYID'high(expr)	Upper-bound of [nth] index
ARYID'low(expr)	Lower-bound of [nth] index
ARYID'range(expr)	left down to right
ARYID'reverse_range(expr)	right down to left
ARYID'length(expr)	Length of [nth] dimension
ARYID'ascending(expr)	right >= left ?
SIGID'delayed(TIME)	Delayed copy of signal
SIGID'stable(TIME)	Signals event on signal
SIGID'quiet(TIME)	Signals activity on signal
SIGID'transaction	Toggles if signal active

SIGID'event	Event on signal ?
SIGID'active	Activity on signal ?
SIGID'last_event	Time since last event
SIGID'last_active	Time since last active
SIGID'last_value	Value before last event
SIGID'driving	Active driver predicate
SIGID'driving_value	Value of driver
OBJID'simple_name	Name of object
OBJID'instance_name	Pathname of object
OBJID'path_name	Pathname to object

#### 7. PREDEFINED TYPES

BOOLEAN	True or false
INTEGER	32 or 64 bits
NATURAL	Integers >= 0
POSITIVE	Integers > 0
REAL	Floating-point
BIT	'0', '1'
BIT_VECTOR(NATURAL)	Array of bits
CHARACTER	7-bit ASCII
STRING(POSITIVE)	Array of characters
TIME	hr, min, sec, ms, us, ns, ps, fs
DELAY_LENGTH	Time >= 0

#### 8. PREDEFINED FUNCTIONS

NOW	Returns current simulation time
DEALLOCATE(ACCESS_TPOBJ)	Deallocate dynamic object
FILE_OPEN(status, FILEID, string, mode)	Open file
FILE_CLOSE(FILEID)	Close file

#### 9. LEXICAL ELEMENTS

Identifier ::= letter { [underline] alphanumeric }  
 decimal literal ::= integer [ . integer ] [ E[+|-] integer ]  
 based literal ::=  
     integer # hexint [ . hexint ] # [ E[+|-] integer ]  
 bit string literal ::= B[IOX] " hexint "  
 comment ::= - comment text

© 1995-2000 Qualis Design Corporation. Permission to reproduce and distribute strictly verbatim copies of this document in whole is hereby granted.

#### Qualis Design Corporation

Elite Training / Consulting in Reuse and Methodology

Phone: +1-503-670-7200 FAX: +1-503-670-0809  
 E-mail: info@qualis.com Web: www.qualis.com

Also available: 1164 Packages Quick Reference Card  
 Verilog HDL Quick Reference Card